

# Analog

EE1205 : Signals and Systems  
Indian Institute of Technology Hyderabad

Chirag Garg  
(EE23BTECH11206)

## I. QUESTION 12.7.4

**Question:** A  $60 \mu\text{F}$  capacitor is connected to a 110 V, 60 Hz ac supply. Determine the rms value of the current in the circuit.